

1. EXAMEN: Rodrigo R. Rubio Haro

Código

```
-- author: Rubio Haro Rodrigo
-- device: 22v10

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
ENTITY coder IS
    PORT (
        E : IN STD_LOGIC_VECTOR (1 DOWNTO 0);-- 2 bits
        Z, Y, sel : IN STD_LOGIC;
        display : OUT STD_LOGIC_VECTOR (6 DOWNTO 0) -- 7 Bits
    );
END coder;
----
ARCHITECTURE arg_coder OF coder IS
    SIGNAL DZ : STD_LOGIC_VECTOR (3 DOWNTO 0);-- 4 Bits
    SIGNAL DY : STD_LOGIC_VECTOR (3 DOWNTO 0);-- 4 Bits
    SIGNAL mux : STD_LOGIC_VECTOR (3 DOWNTO 0);-- 4 Bits

BEGIN

    -- Deco Z
    PROCESS (DZ, E, Z)
    BEGIN
        IF Z = '1' THEN
            IF (E = "00") THEN
                DZ <= "0001";
            ELSIF (E = "01") THEN
                DZ <= "0010";
            ELSIF (E = "10") THEN
                DZ <= "0100";
            ELSE
                DZ <= "1000";
            END IF;
        ELSE
            DZ <= "0000";
        END IF;
    END PROCESS;
```

```
-- Deco Y
PROCESS (DY, E, Y)
BEGIN
    IF Y = '1' THEN
        --Secuencial
        CASE (E) IS
            WHEN "00" =>
                DY <= "0001";
            WHEN "01" =>
                DY <= "0010";
            WHEN "10" =>
                DY <= "0100";
            WHEN "11" =>
                DY <= "1000";
            WHEN OTHERS =>
                DY <= "0000";
        END CASE;
    ELSE
        DY <= "0000";
    END IF;


END PROCESS;

WITH sel SELECT mux <=
    DZ WHEN '0',
    DY WHEN '1',
    "0000" WHEN OTHERS;

-- catodo: prenden con 1
display <= "1001111" WHEN mux = "0000" ELSE -- 0
    "0110000" WHEN mux = "0001" ELSE -- 1
    "1101101" WHEN mux = "0010" ELSE -- 2
    "0110011" WHEN mux = "0100" ELSE -- 4
    "1111111" WHEN mux = "1000" ELSE -- 8
    "0000000";

END arq_coder;
```

Simulación en Galaxy

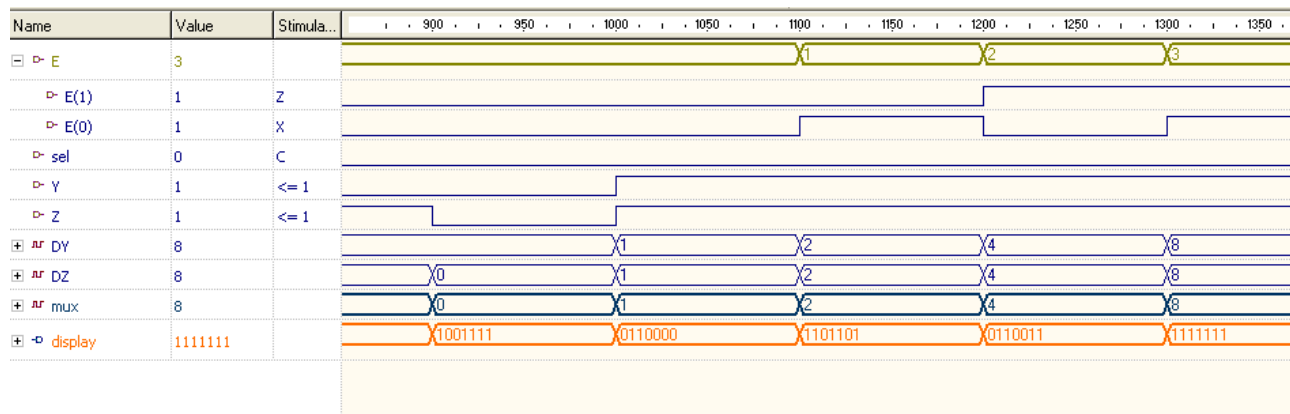

Efectivamente se comprobó la propuesta teórica mediante la simulación de ondas del código VHDL